

## Program-13

**Objective:** To implement 4X2 encoder and 8X3 encoder


### Theory:

The combinational circuits that change the binary information into N output lines are known as Encoders. The binary information is passed in the form of  $2^N$  input lines. The output lines define the N-bit code for the binary information. In simple words, the Encoder performs the reverse operation of the Decoder.

### 4X2 Encoder

#### Truth Table

INPUTS				OUTPUTS	
$Y_3$	$Y_2$	$Y_1$	$Y_0$	$A_1$	$A_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

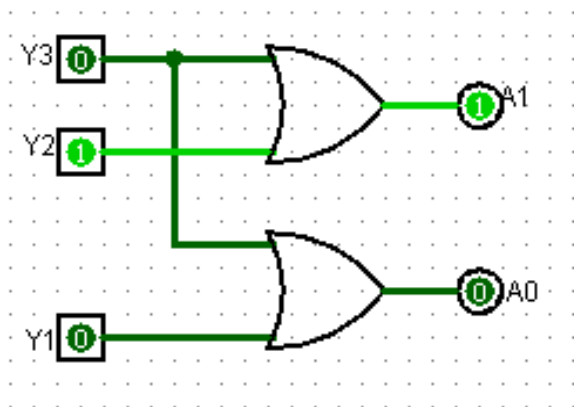

### Expression

$$A_1 = Y_3 + Y_2$$

$$A_0 = Y_3 + Y_1$$

Tarang Priyadarshi  
CSE(AI)  
2100291520057  
**8X3 Encoder**

Truth Table

Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

